

Sessional- I

Branch: CSE

Course Code: BT EE 103A


Course Title: Basic Electrical Engineering

Que. 1

- A) What do you mean by Resonance.
- B) Differentiate between ideal source and practical source.
- C) Draw equivalent circuit of Thevenin's theorem.
- D) Define Quality factor and Form factor.
- E) Distinguish between a phasor and a complex quantity.

Que. 2 In the circuit of Fig., find R and C. Given $V_b = 3V_a$ and V_b and V_a are in quadrature. Find also the phase relation between V, V_b , V_a and I.

Que.3 By using Kirchhoff's laws, find the current in XY in the circuit shown in Figure

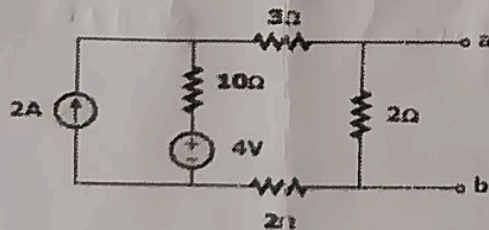

Que.4

Find the Norton equivalents of the following circuit at terminal a-b.

Max Time: 1 Hours

Max Marks: 20

$$I_2 = 160 - I_1$$

